



Education and Training for Corrosion Control

### Intermediate Course

### CHAPTER 7 RECTIFIERS

Appalachian Underground Corrosion Short Course West Virginia University Morgantown, West Virginia

Copyright © 2006



# Safety

• Visually inspect to commercial power service to pole and service mounted on the pole


- Inspect service disconnect and rectifier ground
- Test rectifier case for voltage prior to unlocking or opening
- Follow your company Lock Out Tag Out procedure, if you have to troubleshoot, repair or replace any components

# Transformer/Rectifier Component Review

- **Two distinct operations** 
  - AC Transformer: Allows for the adjustment of the current going to the DC Rectifier element
  - DC Rectifier: Converts the AC current to DC current for application to the cathodic protection system
- Additional components include primary and secondary breakers; lightning protection (AC & DC); filter choke; calibrated shunt; courtesy outlet; and output gauges.


## **AC Transformer**



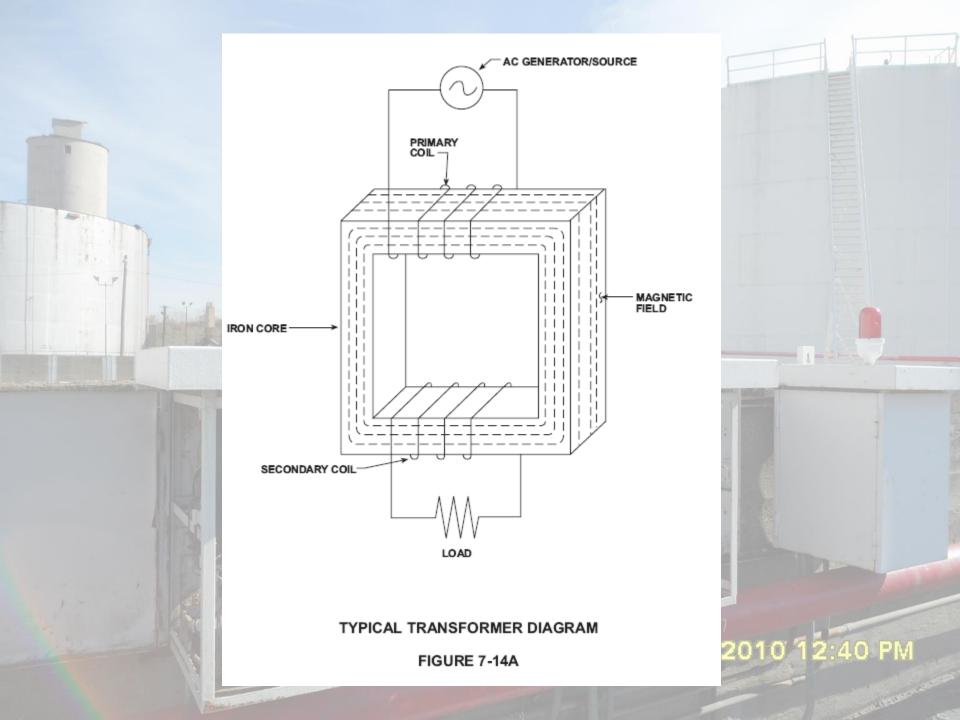


## **DC Rectifier – Diode Stack**

## DC Rectifier – Selenium Stack

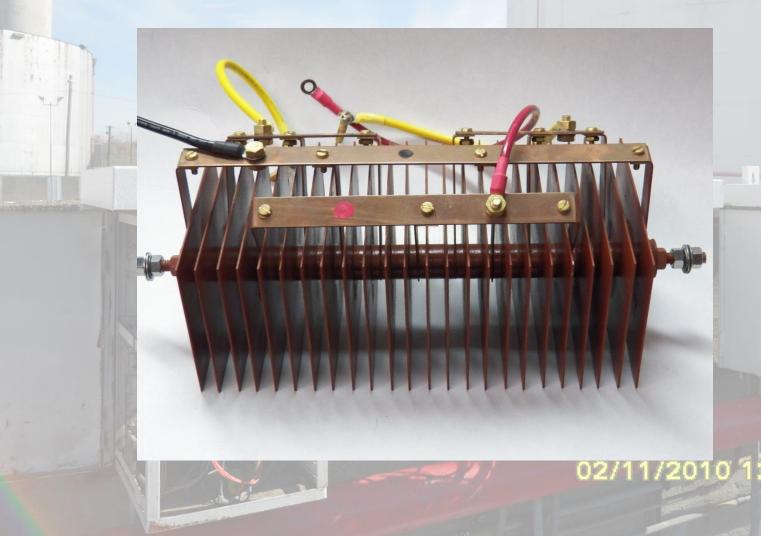


:40 PM



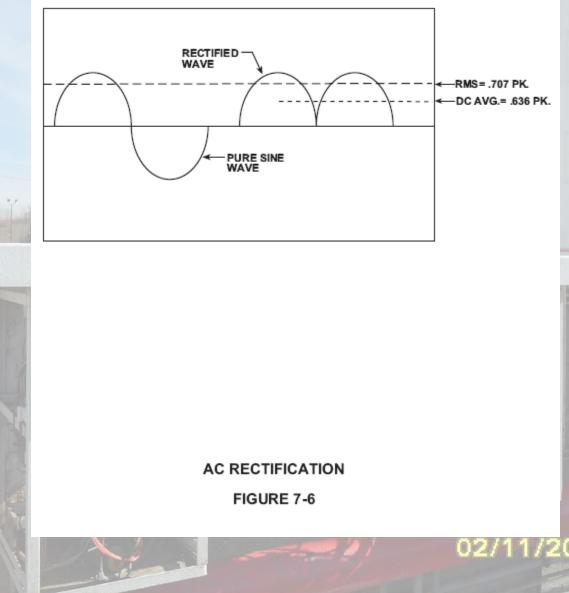




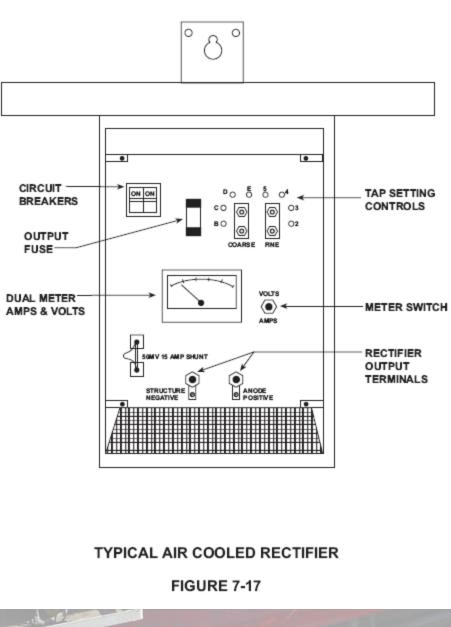


:40 PM 2010



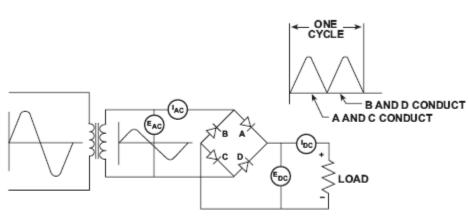

ALTERNATE SCHEMATIC ARRANGEMENT

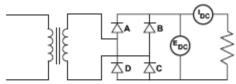


#### SINGLE PHASE BRIDGE CIRCUIT

FIGURE 7-7





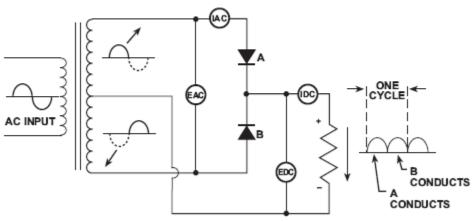


#### SINGLE PHASE CENTER-TAP CIRCUIT


FIGURE 7-8






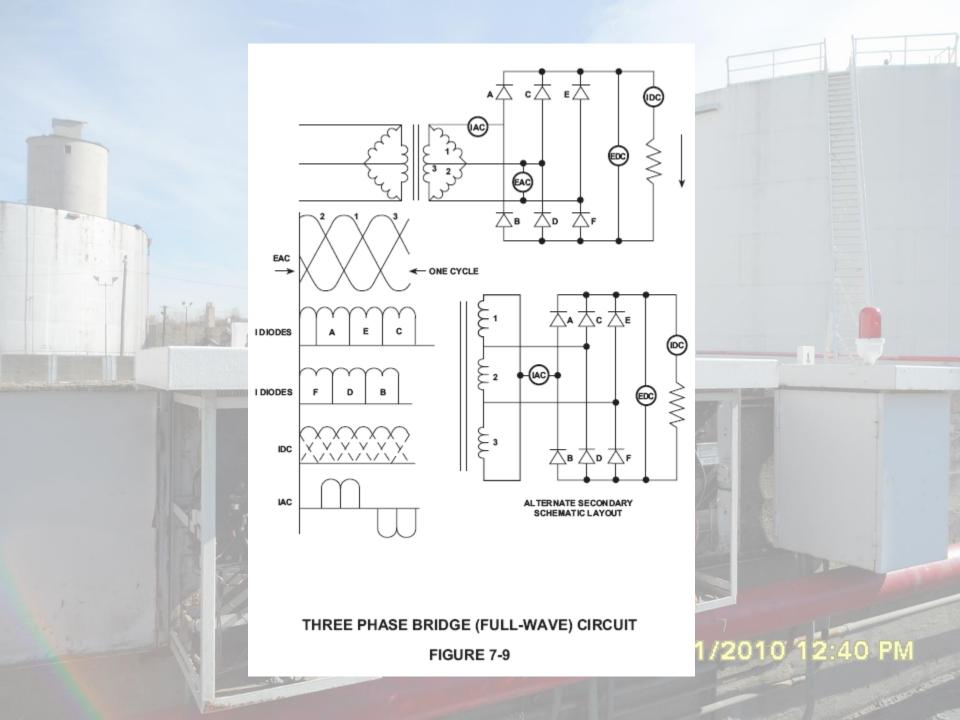




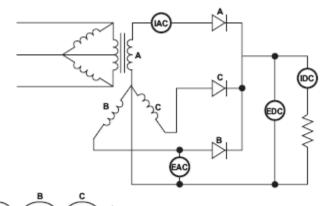

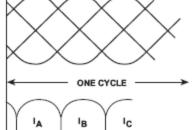



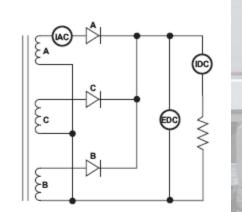


THREE PHASE WYE CIRCUIT

FIGURE 7-10

2010 12:40 PM




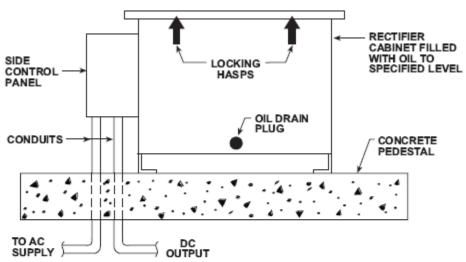

#### TYPICAL OIL COOLED RECTIFIER

FIGURE 7-18



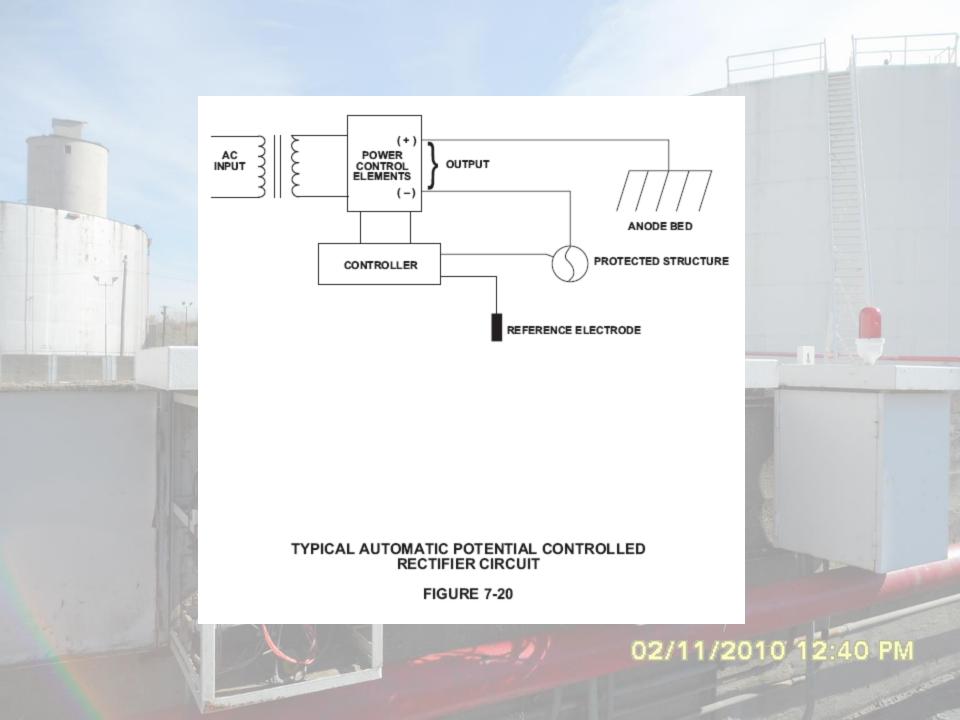

#### 23/06/2011 02:49 PM

-

•

## **Additional Components**

- Lightning Arrestors both AC & DC I/O
- Filter Chokes Clean up or smooth out DC
- Fuses & Breakers protect components against unexpected faults
- Calibrated Shunt provides a means to accurately measure the DC cathodic protection current output

02/11/2010

 Courtesy Outlet – AC power for test equipment (interrupters)

# Transformer/Rectifier Function

- AC current comes in from the power supply then through a primary breaker to the transformer via the taps or rheostat
- From the transformer the AC continues to the rectifying element where AC is converted to DC current
- The DC current then flows via the shunt to the cathodic protection outputs (structure & anodes)

02/11/2010

- SAFETY is often the most disregarded, but most important aspect of performing rectifier maintenance
  - Use proper safety practices and equipment
  - Use common sense & trust your senses
  - Establish safe work habits
- DOT regulated systems require transformer/rectifiers to be inspected every 60 days

02/11/2010

# Remote Monitoring Units (RMUs)

- The use of RMUs are a very effective means to monitor the transformer/rectifier I/O.
- However, this does <u>not</u> alleviate the need to periodically visit each location to visually inspect and perform PM tasks.




- 1. Record transformer rectifier I/O & settings using both a calibrated DVOM & the meters.
  - **1.** Check and adjust meters using the DVOM to calibrate
- 2. Turn OFF the AC power supply!
  - 1. AC feed, not the transformer/rectifier.
  - 2. Verify the power to the transformer/rectifier is off using the DVOM.
- 3. Feel components for excessive heat. Use caution.
- 4. Visually inspect components for damage.
  - 1. Lighting strike, surge, short, etc.


- 5. Clean, inspect & tighten connections.
  - 1. This includes cleaning the tap bars and the structure & anode connections.
- 6. Clean all components with a non-metallic brush (old paint brush).
  - 1. Air screen, panel, transformer and rectifying element
  - 2. Plug any extraneous openings
- 7. Repair or replace damaged connections or insulated wires.
- 8. Evaluate oil cooled units fluid level and cleanliness.

9. Evaluate protective devices.
1. Fuses, lightning arrestors, breakers, etc.
2. If defective or unsure, replace the component with equivalent
10. Recheck settings and re-energize the AC to the transformer/rectifier.
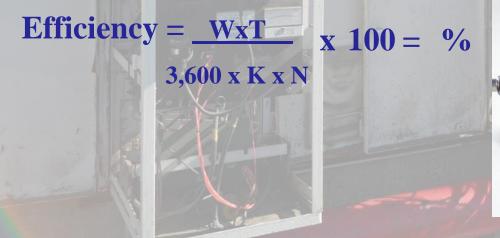
### **Rectifier Efficiency**

 $\frac{60 \text{ min }_{x}60 \text{ sec }_{=} 3,600 \text{ sec/hr}}{1 \text{ hr } 1 \text{ min}}$   $K \text{ watt-hr, N rev, T sec, } E_{DC}, I_{DC}$   $E_{DC} \times I_{DC} = \text{Watts}$ 



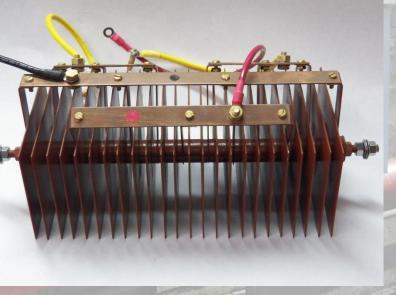

### **Rectifier Selection**

There are several requirements that must be considered for the proper selection of a cathodic protection transformer/rectifier.

Selection of a transformer/rectifier should be made by a qualified corrosion engineer.



### 02/11/2010 12:40 PM

11.50 AM

11.0

10)

50 M.W

3 4

-

Anna

C, INC. RADO VASKA SP

### 02/11/2010 12:40 PM

AND

11

01-

AP S X

-

